


Lab Assignment 1: Solving Systems of Linear Equations Describing Electrical Circuits

Your full name: Xu Ji

Your utorID: 1008784406

A more complex circuit

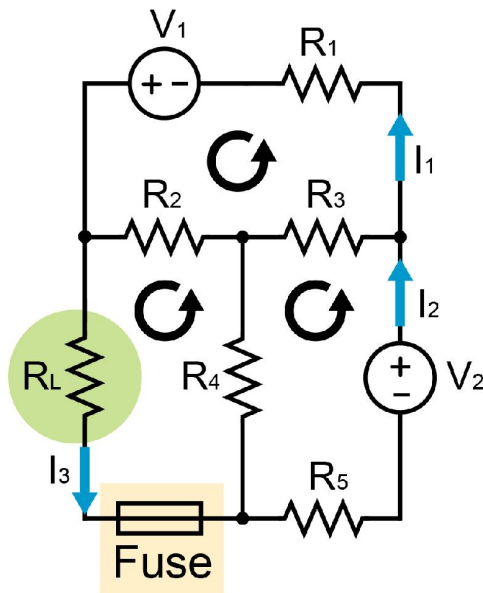Consider the following circuit with a variable resistor R_L :



We can construct a system of equations to describe this circuit using a combination of KVL and KCL:

top loop: $V_1 - R_2(I_1 - I_3) + R_3(I_2 - I_1) - R_1I_1 = 0$

left loop: $-R_LI_3 - R_4(I_3 - I_2) + R_2(I_1 - I_3) = 0$

outmost loop: $V_1 - R_LI_3 - R_5I_2 + V_2 - R_1I_1 = 0$

Problem 1: Finding the minimum resistance to keep the fuse intact

The fixed circuit parameters are defined here for you.

Resistors:

```
R1 = 8; R2 = 4; R3 = 4; R4 = 6; R5 = 1; % Units: Ohms
```

Voltage sources:

```
V1 = 120; V2 = 120; % Units: Volts
```

What must the variable resistor (R_L) be set to in order to prevent a 5 Amp fuse from melting?

- Tell MATLAB to display the value for R_L to 1 decimal place using fprintf and matrix indexing.
- eg. you should be getting this value directly from a variable in memory

Hint: Include the unknown resistance as a variable in your system of equations.

eg. $x = \begin{bmatrix} I_1 \\ I_2 \\ R_L \end{bmatrix}$

```
I3 = 5; % unit: ampre
A = [-R1 - R2 - R3, R3, 0; R2, R4, -I3; -R1, -R5, -I3];
b = [-V1 - R2 * I3; R4 * I3 + R2 * I3; -V1 - V2]; % constructs an augmented matrix for
x = linsolve(A, b); % solves the augmented matrix into RREF form
final_answer = x(3); % stores the required element
fprintf('The minimum R_L to prevent melting the fuse is %.1f Ohms', final_answer)
```

The minimum R_L to prevent melting the fuse is 22.9 Ohms

Problem 2: Using a for loop to approximate the answer

In many real life scenarios, an numerical estimate is often adequate for most engineering applications, especially because it may not be feasible to compute an exact solution.

Use a for-loop to solve this circuit for varying values of R_L to find the resistance in R_L that will lead to excessive current through the fuse.

- Test values of R_L between 0 and 50 Ohms, in steps of 0.5 Ohms
- Save the resultant current that would be going through the fuse
- Print the value of R_L that will cause the 5 Amp fuse to melt

Hints:

- In this part, we need to reconstruct our system of equations.
- Now, our unknowns will be I_1, I_2 , and I_3 . We compute the value of I_3 given a some value for R_L .

```
RList = []; % saves all the tested resistance (RL)
IList = []; % saves all the respective current through fuse (I3)
LastR = 0; % sets initial value for RL, unit: Ohm
fuse_intact = false; % flag used to indicate if the fuse is melted
for RL = 0 : 0.5 : 50 % for loop with base 0, step 0.5, ends at RL = 50
```

```

A = [-R2 - R3 - R1, R3, R2; R2, R4, -RL - R4 - R2; -R1, -R5, -RL];
b = [-V1; 0; -V1 - V2]; % implements an augmented matrix for the loop
x = linsolve(A, b); % solves the augmented matrix into RREF form
I3 = x(3); % slices the vector to get I3
RList(end + 1) = RL; % appends the tested resistance to list
IList(end + 1) = I3; % appends the respective current to list
if fuse_intact == false && I3 <= 5 % only enters the branch when the first RL value
    Rout = LastR; % stores the output value for future
    fuse_intact = true; % toggles flag
end
LastR = RL; % updates the LastR value
end
fprintf('The maximum resistance that leads to the melting of the fuse is %.1f Ohms', Rout);

```

The maximum resistance that leads to the melting of the fuse is 22.5 Ohms

Generate a scatter plot of your simulation:

- Show the variable resistance on the x-axis and the resultant current through the fuse on the y-axis
- Include a horizontal line indicating the maximum current of the fuse
- Remember to label your plot axes and add a plot title

Hint: The following commands may be useful.

```

title('This is my title') % Set the title for the active axis
xlabel('My label'), ylabel('My label') % Set the label on the corresponding axis


plot(x, y) % plot the values of x and y as a line plot
scatter(x, y) % plot the values of x and y in a scatter plot
xline(x), yline(y) % draw a vertical / horizontal line at the specified value

```

```

plot(RList, IList) % plots the graph with elements in RList as independent variable, e
ylines(5) % indicates the maximum current in the fuse
title('I3 over RL Graph') % labels the title of the graph
xlabel('RL / Ohm'), ylabel('I3 / Ampere') % labels the y, x axes

```

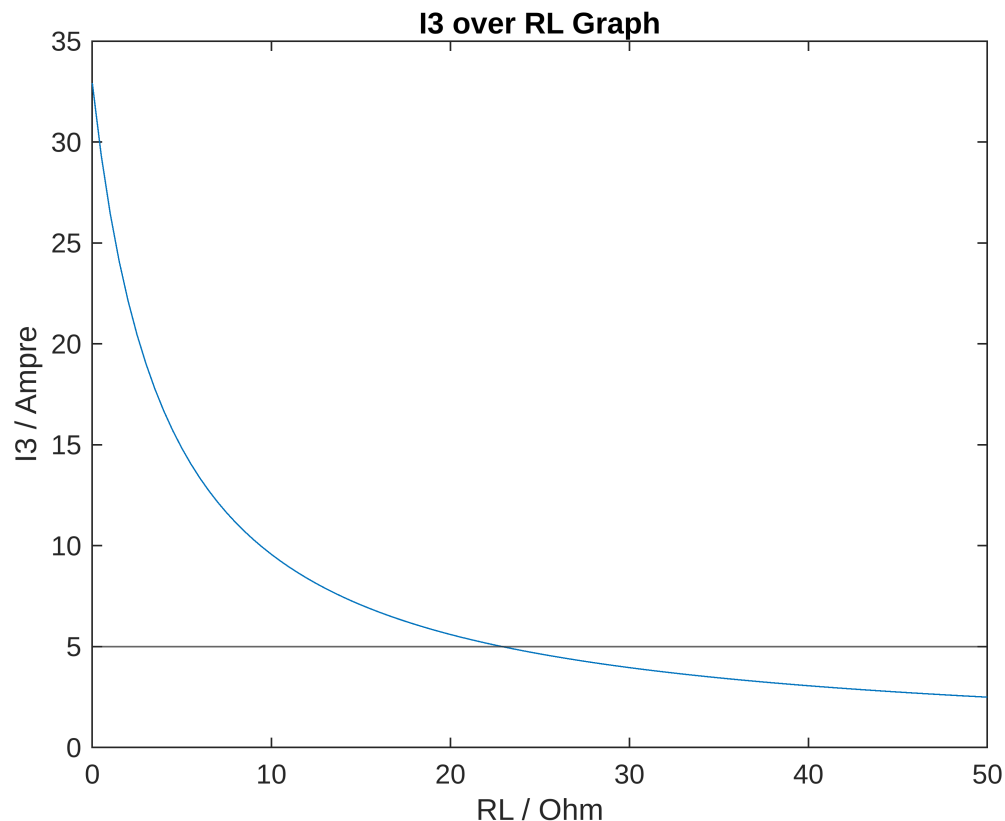

Problem 3: Simulating the current through I_2 as the fuse melts

When a fuse melts, it completely interrupts the flow of current through the circuit at that point.

Imagine an experimenter set-up this circuit in the lab, with the variable resistor (R_L) initially set to 50 Ohms, and a fuse that will melt above 5 Amps. The experimenter gradually reduce the resistance in the resistor until it reaches 0 Ohms. **Plot the current I_2 against the resistance in R_L as the resistor is adjusted from 50 Ohms down to 0 Ohms.**

Hints:


- Start by copying the for-loop you wrote for Problem 2B above.
- You may need to solve the circuit twice in the for-loop: once to determine if the fuse will melt, and once again to solve the circuit accounting for if the fuse is melted.

```
RList = []; % saves all the tested resistance (RL)
IList = []; % saves all the respective current through fuse (I3)
fuse_intact = true; % flag used to indicate if the fuse is melted
for RL = 50 : -0.5 : 0 % for loop with base 50, step -0.5, ends at RL = 0
    A = [-R2 - R3 - R1, R3, R2; R2, R4, -RL - R4 - R2; -R1, -R5, -RL];
```

```

b = [-V1; 0; -V1 - V2]; % implements an augmented matrix for the loop when the fuse
x = linsolve(A, b); % solves the augmented matrix into RREF form
I3 = x(3); % slices the vector to get I3
I2 = x(2); % assume fuse is intact, slices the vector to get I3
if fuse_intact == true % if the fuse is not melted yet
    if I3 <= 5 % if current will not melt the fuse
        RList(end + 1) = RL; % appends the tested resistance to list
        IList(end + 1) = I2; % appends the respective current to list
    else % when the fuse is melted for the first time
        fuse_intact = false; % toggles flag
        C = [-R2 - R3 - R1, R3; R3, -R3 - R4 - R5];
        d = [-V1; -V2]; % implements an augmented matrix for the loop when the fuse
        y = linsolve(C, d); % solves the augmented matrix into RREF form
        I2 = y(2); % slices the vector to get I2
        RList(end + 1) = RL; % appends the tested resistance to list
        IList(end + 1) = I2; % appends the respective current to list
    end
else % when the fuse is already melted
    C = [-R2 - R3 - R1, R3; R3, -R3 - R4 - R5];
    d = [-V1; -V2]; % implements an augmented matrix for the loop when the fuse is
    y = linsolve(C, d); % solves the augmented matrix into RREF form
    I2 = y(2); % slices the vector to get I2
    RList(end + 1) = RL; % appends the tested resistance to list
    IList(end + 1) = I2; % appends the respective current to list
end
end
plot(RList, IList) % plots the graph with elements in RList as independent variable, el
title('I2 over RL Graph') % labels the title of the graph
xlabel('RL / Ohm'), ylabel('I2 / Ampere') % labels the y, x axes

```

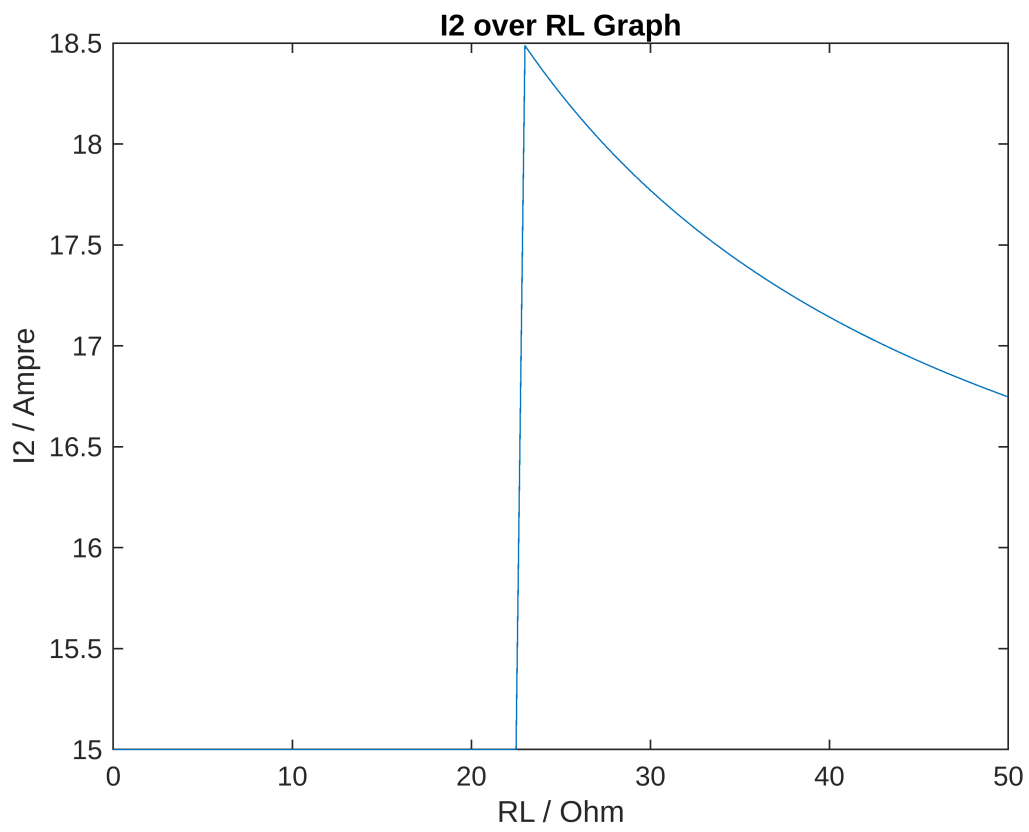

Submission instructions

1. Ensure the final results for each problem are displayed (use statements without a semicolon or use the `disp`, `fpr`, `display` commands)
2. Run the script from beginning to end to check all your code
3. Export your solutions as a PDF and **upload both MLX and PDF files** to Quercus

